



Submit Project # 1 Reports Next Week

- **Read the Project # 1 Deliverables document**
- **Priorities in lab today**
 1. Verify Project # 1 with Template resistor values
 2. Insert your resistor values in theoretical & measured sections
 3. Project # 1 Excel file
 - Clear values in the measured columns
 4. Build circuit and measure R_{th} , V_G , and V_{th}
 - % difference R_{th} and V_{th} should be $\leq \approx 1-2\%$
 - Resolve problems before proceeding
- **Reclaim your resistors for Project # 1**
- **MATLAB = verify measured data before you leave**
- **Questions ?**



Project # 1

- Pre-lab = Read project & tutorial + the following:
 - **MATLAB code working properly & verify your measurements**
 - Run simulation => Compare with solution
 - 1) Use standard values => use values below for **initial simulation**
 - 2) Then use your selected values
 - Final lab values => $500\ \Omega \leq R_n \leq 2\ \text{k}\Omega$, $n = \{1, 2, 3, \dots, 8, 10\}$
 - (Required) MATLAB “Publish” for your documents
 - R_1 through $R_8 < R_{10}$, and R_9 is variable



- Decade Resistance Box
 - Use as R_9 when making measurements
- Measurements today

Setup global variables

```
% These element values are fixed in the circuit.
VG = 12;           % Generator voltage
R1 = 1000;         % Ohms
R2 = 1000;         % Ohms
R3 = 1000;         % Ohms
R4 = 500;          % Ohms
R5 = 500;          % Ohms
R6 = 500;          % Ohms
R7 = 500;          % Ohms
R8 = 1000;         % Ohms
R10 = 500;         % Ohms

% This element value is the R9 variable in the circuit.
R9 = [1:10:10^5]; % Ohms
```




Project # 1

- **MATLAB code design (3 files => script & functions)**
 - Template code has been provided
 - You will fill in the missing code sections
 - **MATLAB Publish must be Word Document format**
 - Required approach
 - MATLAB Publish + Measurements + Hand calculations
 - Answer the questions in the Deliverables document
 - Verify your code is working properly with TA
 - Use Excel blank template to record measurements
 - Take Measurements in lab today
 - Plotting: use MATLAB **semilogx()** and **makedatatip()**



Measure all resistors first

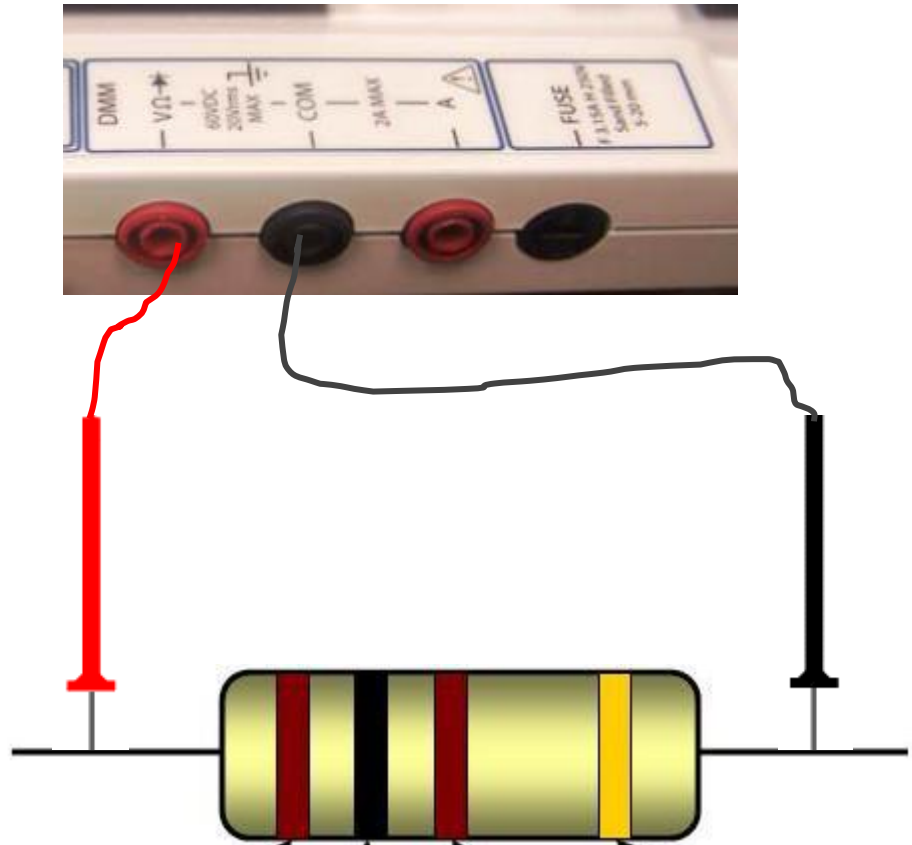






Measuring R_{TH}

Turn off the
Prototyping Board
Power Switch to
disable VPS's


Disconnect R9 and
the VPS. Then put
a short in place of
the VPS.

Connect the
Ohm meter

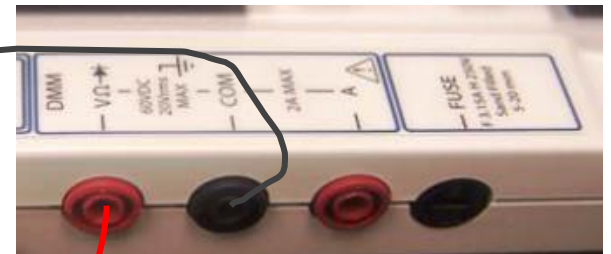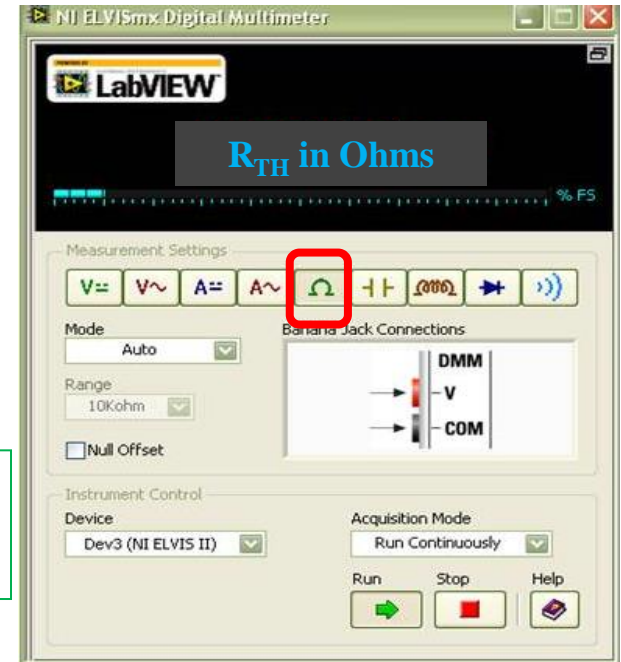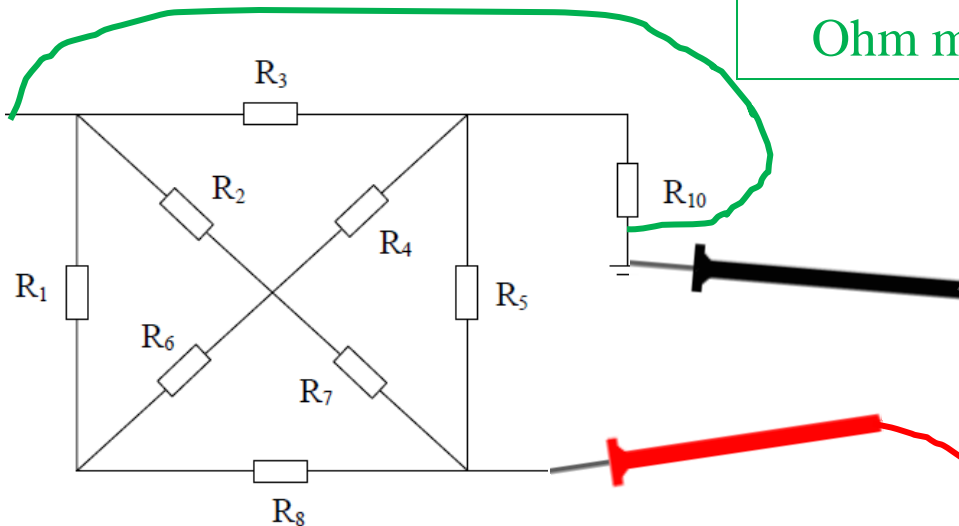





Measuring V_{TH}

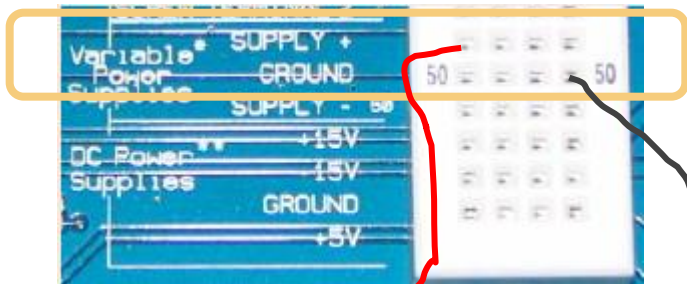

Turn on the
Prototyping Board
Power Switch.


Disconnect R9
and connect the
VPS = +12V.

Connect the
Volt meter

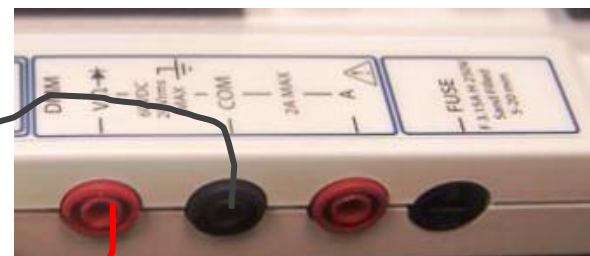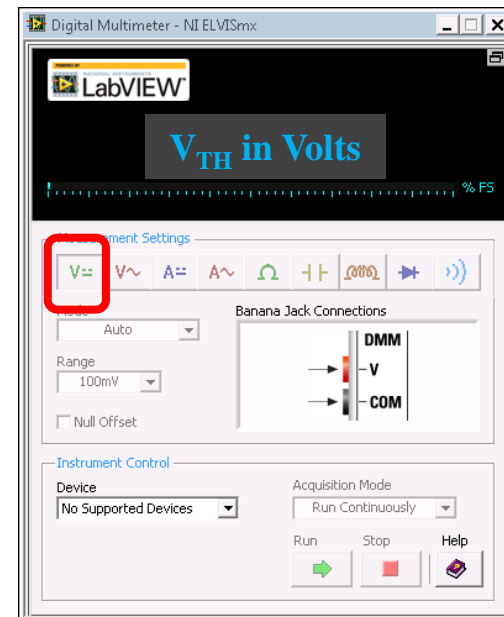




Full circuit configuration

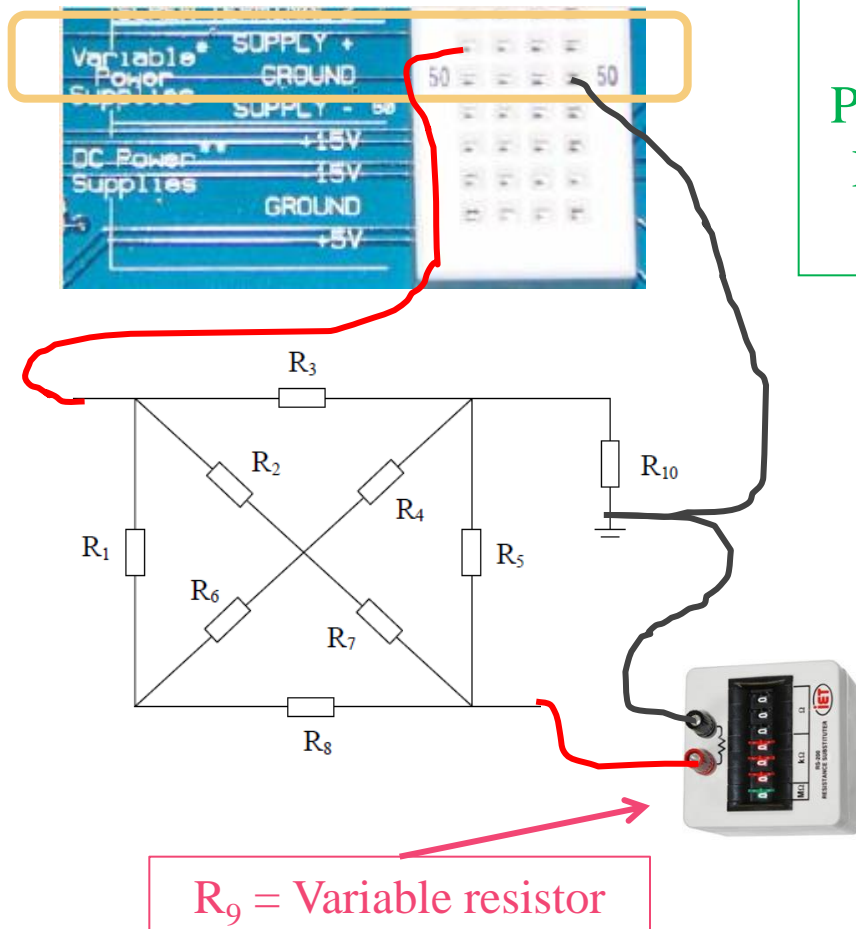

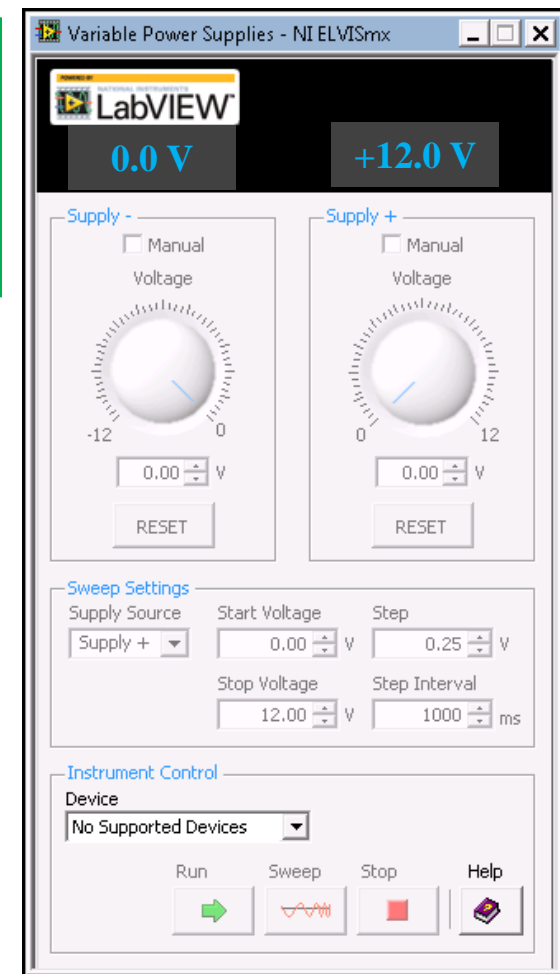Turn on the
Prototyping Board
Power Switch to
enable VPS's





SANTA CLARA UNIVERSITY

Project # 1

MATLAB Verification

